

# Analogue Electronics

## Experiment 2 - MOSFET Characteristics

### ENG221

Shane REYNOLDS

October 31, 2019

Date Performed: April 8, 2015  
Instructor: Dr Sina Vafi

## 1 Objective

To determine the internal parameters of a MOSFET.

### 1.1 Background

**Output Resistance in Saturation** In saturation, the idealised model of the MOSFET tells us that  $i_D$  is independent of  $v_{DS}$ . This implies that some change  $\Delta v_{DS}$  means that there is no change in  $i_D$ , however, this is an idealisation. In reality the device will experience something called channel length modulation. This shrinkage of the length of the channel means that the MOSFET is now modelled by:

$$i_D = \frac{1}{2}k'_n \left( \frac{W}{L} \right) (v_{GS} - V_t)^2 (1 + \lambda v_{DS}) \quad (1)$$

where

$i_D$  = current through the device

$\frac{W}{L}$  = ratio of the device width to the device length

$k'_n$  = transconductance parameter

$v_{GS}$  = voltage from the gate to the source

$V_t$  = threshold voltage

$\lambda$  = channel length modulation parameter

$v_{DS}$  = the voltage from the drain to the source

In equation (1) we see that  $i_D$  is linearly dependent on  $v_{DS}$ . Extrapolating the model in saturation yields the following formula:

$$V_A = \frac{1}{\lambda} \quad (2)$$

If  $i_D$  is now dependent on  $v_{DS}$ , then for a given  $v_{GS}$ , a change  $\Delta v_{DS}$  yields a change  $\delta i_D$  in the drain current  $i_D$ . Hence we define the output resistance as  $r_o$  and express it as:

$$r_o = \left[ \frac{\partial i_D}{\partial v_{DS}} \right]_{v_{GS} \text{ constant}}^{-1} \quad (3)$$

## 2 Experimental Data

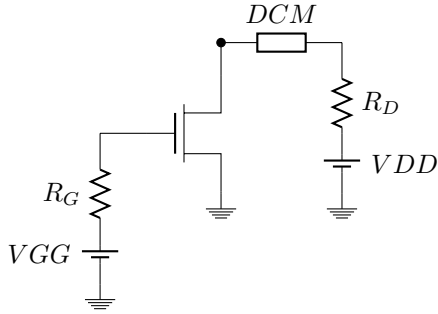


Figure 1: n-type MOSFET circuit

$V_{DD}$	$V_{GG}$	$V_{R_D}$	$V_{R_D}/R_D$	$V_D$
10.00 V	1.3 V	0 V	0 mA	10.00 V
10.00 V	2.00 V	0.38 V	0.38 mA	9.62 V
8.00 V	2.00 V	0.38 V	0.38 mA	9.62 V
6.00 V	2.00 V	0.38 V	0.38 mA	9.62 V
4.00 V	2.00 V	0.38 V	0.38 mA	9.62 V
2.00 V	2.00 V	0.38 V	0.38 mA	9.62 V
10.00 V	3.00 V	1.58 V	1.58 mA	8.42 V
8.00 V	3.00 V	1.58 V	1.58 mA	8.42 V
6.00 V	3.00 V	1.58 V	1.58 mA	8.42 V
4.00 V	3.00 V	1.58 V	1.58 mA	8.42 V
2.00 V	3.00 V	1.36 V	1.36 mA	8.64 V
10.00 V	4.00 V	3.48 V	3.48 mA	6.52 V
8.00 V	4.00 V	3.48 V	3.48 mA	6.52 V
6.00 V	4.00 V	3.48 V	3.48 mA	6.52 V
4.00 V	4.00 V	3.48 V	3.48 mA	6.52 V
2.00 V	4.00 V	2.51 V	2.51 mA	7.49 V
10.00 V	5.00 V	5.56 V	5.56 mA	4.40 V
8.00 V	5.00 V	5.56 V	5.56 mA	4.40 V
6.00 V	5.00 V	5.56 V	5.56 mA	4.40 V
4.00 V	5.00 V	5.20 V	5.20 mA	4.80 V
2.00 V	5.00 V	3.33 V	3.33 mA	6.67 V

Table 1: Output characteristic

$V_{DD}$	$V_{GG}$	$V_{R_D}$	$V_{R_D}/R_D$	$V_D$
10.50 V	5.00 V	5.5 V	5.5 mA	5 V
15.6 V	5 V	5.56 V	5.56 mA	10 V

Table 2: Output resistance

$v_{GS}$	$i_D$
1.3 V	10 mA
1.4 V	40 mA
1.5 V	70 mA
1.6 V	110 mA
1.7 V	140 mA
2.0 V	360 mA
3.0 V	1560 mA
4.0 V	3240 mA
5.0 V	3710 mA

Table 3: Control  $V_{DD} = 5V$

$v_{GS}$	$i_D$
1.3 V	20 mA
1.4 V	30 mA
1.5 V	50 mA
1.6 V	80 mA
1.7 V	130 mA
2.0 V	320 mA
3.0 V	670 mA
4.0 V	740 mA
5.0 V	780 mA

Table 4: Control  $V_{DD} = 1V$

$v_{GS}$	$i_D$
1.3 V	10 mA
1.4 V	30 mA
1.5 V	70 mA
1.6 V	100 mA
1.7 V	150 mA
2.0 V	390 mA
3.0 V	1610 mA
4.0 V	3350 mA
5.0 V	5460 mA

Table 5: Control  $V_{DD} = 10V$

## 3 Calculations

### 3.1 Output Resistance

In the second task we are asked to find the resistance to which the characteristic slope corresponds. According to equation (3) we see that the output resistance is the inverse of the slope of the  $i_D$ - $v_{DS}$  line when operating in the saturation region. Hence from equation (3), for a given  $v_{GS}$  we can say that:

$$r_o = \frac{\Delta v_{DS}}{\Delta i_D}$$

Using the experimental data in table 2 we see that:

$$\begin{aligned} r_o &= \frac{10 - 5}{5.56\text{E-}3 - 5.5\text{E-}3} \\ &= 83.88\text{k}\Omega \end{aligned}$$

Now the drain to source was shunted with a resistor of magnitude 83.33 k $\Omega$ . The previous change in current was:

$$\Delta i_{D_1} = 5.56\text{mA} - 5.5\text{mA} = 0.06\text{mA}$$

The change in current with the shunt added was:

$$\Delta i_{D_2} = 5.62\text{mA} - 5.56\text{mA} = 0.06\text{mA}$$

Now, if  $V_G = V_{DS} = 5\text{V}$ , then the shunt resistor should be the same value as above: 83.33 k $\Omega$ . This is because  $V_G$  is unchanged. The theory outlined in the background tells us that provided the device is operating in saturation, for some given  $V_G$ , then  $i_D$  and  $v_{DS}$  are linearly related. This means that the slope is constant, which in turn implies that the output resistance is constant for a given  $V_{GS}$ .

Now to determine  $V_A$  and  $\lambda$  we need to determine the equation of the linear relation between  $i_D$  and  $v_{DS}$ . The slope is simply the inverse of the resistance, hence:

$$i_d = \frac{1}{83.33\text{E}3} v_{DS} + \text{constant}$$

To find the constant, we can use the tuple  $(i_D, v_{DS}) = (5.56\text{mA}, 10\text{V})$ :

$$\begin{aligned} 5.56\text{mA} &= \frac{1}{83.33\text{E}3} \times 10\text{V} + \text{constant} \\ \text{constant} &= 46.33 \end{aligned}$$

Hence the equation is:

$$i_d = \frac{1}{83.33\text{E}3} v_{DS} + 46.33$$

Setting  $i_D = 0$  and solving for  $v_{DS}$  will give us the value for  $V_A$ . Hence:

$$V_A = 3860678V$$

Finally, using equation (2) we can solve for the channel length modulation parameter,  $\lambda$ :

$$\lambda = \frac{1}{V_A} = \frac{1}{3860678} = 2.59E-7$$

### 3.2 Control Characteristics

To find the device parameters  $k_n$  and  $V_t$ , we consider two of the experimental data points in table 3. The two points, give us two distinct instances of equation (1), where the modulation parameter,  $\lambda$ , is assumed to be zero. Now, the equations are:

$$i_{D_1} = \frac{1}{2}k'_n(V_{GS_1} - V_t)^2 \quad (4)$$

$$i_{D_2} = \frac{1}{2}k'_n(V_{GS_2} - V_t)^2 \quad (5)$$

If we divide equation (4) by equation (5) we get:

$$\frac{i_{D_1}}{i_{D_2}} = \frac{\frac{1}{2}k'_n(V_{GS_1} - V_t)^2}{\frac{1}{2}k'_n(V_{GS_2} - V_t)^2}$$

Cancelling the  $\frac{1}{2}k'_n$  from the numerator and denominator, we get:

$$\frac{i_{D_1}}{i_{D_2}} = \left( \frac{V_{GS_1} - V_t}{V_{GS_2} - V_t} \right)^2$$

With some algebraic manipulation we arrive at the following relationship:

$$V_T = \frac{\sqrt{\frac{i_{D_1}}{i_{D_2}}} V_{GS_2} - V_{GS_1}}{(\sqrt{\frac{i_{D_1}}{i_{D_2}}} - 1)}$$

Using the two points (1.3V, 20mA), and ((3V, 670mA)), we get:

$$V_T = 0.944V$$

Hence, we can now solve for  $k_n$ :

$$k_n = \frac{2i_D}{(V_{GS} - V_T)^2} = 315.6 \frac{\text{mA}}{\text{V}^2}$$

## 4 Results and Conclusions

### 4.1 Output Resistance

The value which was calculated from the experimental data for the output resistance was  $83.33\text{k}\Omega$ . The value for  $V_A$  is  $3860678\text{V}$  which is very large and consequently the value found for  $\lambda$ ,  $2.59\text{E-}7$ , is very small. The value for  $V_A$  is most likely incorrect as comparable circuits operate with  $V_A$  which is many orders of magnitude smaller than the one calculated. The values of both  $V_A$  are artefacts of the value chosen for shunt resistor.

The shunt resistor values was matched to the output resistance  $r_o$ , but this is very large when compared to the value of the resistance  $R_D$  in the circuit, despite providing the same incremental change in device current  $i_D$ . The selection of the shunt resistor (and even the value of the output resistance) are most likely erroneous. This is due to misconception and lack of understanding with respect to the fundamental operation of the circuit and how to derive the underlying parameters of the device.

### 4.2 Control Characteristics

The experimental data from table 3, 4 and 5 was plotted in Matlab and can be seen in figures 2, 3 and 4 respectively. The values of  $V_t$  that was estimated was  $0.944\text{V}$  and the value of  $k_n$  that was estimated using  $V_t$  was  $315.6 \frac{\text{mA}}{\text{V}^2}$ . The value for  $V_t$  is significantly greater than the standard  $25\text{ mV}$  and hence the calculated value for  $V_t$  and  $k_n$  is most likely in error.

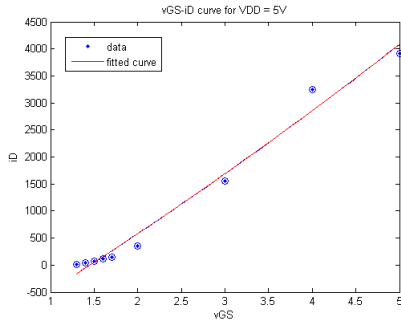


Figure 2: Plot of  $v_{GS}$  vs.  $i_D$  for  $V_{DD} = 5\text{V}$

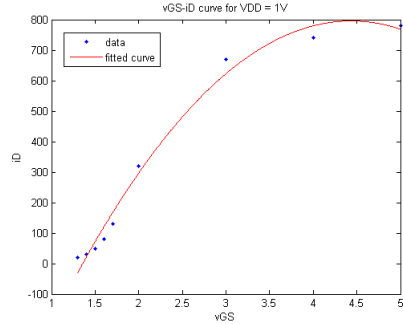


Figure 3: Plot of  $v_{GS}$  vs.  $i_D$  for  $V_{DD} = 1\text{V}$

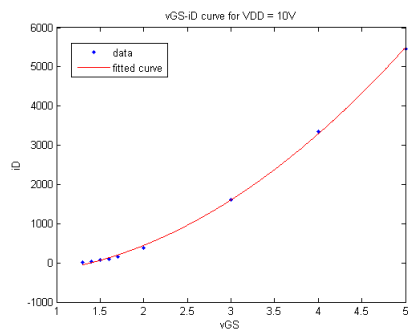


Figure 4: Plot of  $v_{GS}$  vs.  $i_D$  for  $V_{DD} = 10V$